



American International University – Bangladesh

Faculty of Engineering – Electrical & Electronics Engineering

Make sure to add the following table and questions with your assignment as your cover page.

| | | | |
|---------------|-------------------------------------|--------------|----------|
| Course Name : | Microprocessor and Embedded Systems | Course Code: | EEE 4103 |
| Semester : | Fall 24-25 | Section: | M |

| | |
|-----------------|--|
| Assignment No : | 1 (individual submission consisting of 30 marks) |
|-----------------|--|

| | | | |
|---------------|---------------|-------------|------------|
| Student Name: | MD Abdul Aziz | Student ID: | 22-47013-1 |
|---------------|---------------|-------------|------------|

| | | | |
|------------------|------------|----------------------|--------------------|
| Submission Date: | 30-01-2025 | Submission deadline: | Day of final exam. |
|------------------|------------|----------------------|--------------------|

Submission link: <https://forms.office.com/r/TriiTgFhdC>

Answer all questions given below, each question contains **3 marks**

- 1) Design a **n-bit** Adder/ Subtractor circuit, where collect the value from your ID , consider ID is XX-XXXX**n**-X.
- 2) If your ID is XX-XX**ABC**-X, then explain the working principle of bus organization where the number of registers is **Y=A+B+C** in a micro-operation $R1=R2-R0+5$.
- 3) Now, based on question number 2, design and explain the working process of scratchpad memory and a two-port memory system.
- 4) Explain the process of control logic design including all steps for a signed addition function only.
- 5) Explain the process of control logic design including all steps for a signed subtraction function only.
- 6) Deduce a flowchart and microinstruction table for counting the number of 1's in register **R_A** and storing the count in register **R_B**. Include the values of A and B from your ID if it is XX-XXXX**AB**-X.
- 7) Deduce a flowchart and microinstruction table for counting the number of 0's in register **R_A** and storing the count in register **R_B**. Include the values of A and B from your ID if it is XX-XXXX**AB**-X.



American International University – Bangladesh

Faculty of Engineering – Electrical & Electronics Engineering

8) For the processor unit with 16-bit control word variable as in table below, deduce the control words (using table from question no 10) for the following listed micro-operations:

| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 |
|---|---|---|---|---|---|---|---|---|----|----|----|-----|----|----|----|
| A | | | B | | | D | | | F | | | Cin | H | | |

i) $R2 \leftarrow SHL (R3 \text{ OR } R6)$

ii) $R4 \leftarrow 1$

iii) $R3 + \overline{R5} + 1$

iv) $R4 \leftarrow \text{input}$

v) $R4 \leftarrow CLC R2$

9) Design a 4-bit shifter from the given table of question number of 10.

10) Design a 4-bit ALU using table below [consider A & B as ALU source selection, F as the ALU function selection, D as the destination selection and H as shift operation selection variables]

| Binary Code | Function of selection variables | | | | | |
|-------------|---------------------------------|------------|---------------------|---------------------|------|----------------------------|
| | B | A | F with $C_{in} = 0$ | F with $C_{in} = 1$ | D | H |
| | | | | 1 | | |
| 000 | Input Data | Input Data | A-1 | A | None | - |
| 001 | R1 | R1 | A-B-1 | A-B | R1 | No shift |
| 010 | R2 | R2 | A+B | A+B+1 | R2 | Circulate-Right with Carry |
| 011 | R3 | R3 | A | A+1 | R3 | 0's to the output Bus |
| 100 | R4 | R4 | A' | A' | R4 | Shift Right with $I_R = 0$ |
| 101 | R5 | R5 | A XOR B | A XOR B | R5 | Shift Left with $I_L = 0$ |
| 110 | R6 | R6 | A U B | A U B | R6 | Circulate-Left with Carry |
| | R7 | R7 | $A \cap B$ | $A \cap B$ | R7 | 1's to the output Bus |