



American International University – Bangladesh

Faculty of Engineering – Electrical & Electronics Engineering

Make sure to add the following table and questions with your assignment as your cover page.

Course Name :	Microprocessor and Embedded Systems	Course Code:	EEE 4103
Semester :	Fall 24-25	Section:	M

Assignment No :	1 (individual submission consisting of 30 marks)
-----------------	--

Student Name:	MD Abdul Aziz	Student ID:	22-47013-1
---------------	---------------	-------------	------------

Submission Date:	30-01-2025	Submission deadline:	Day of final exam.
------------------	------------	----------------------	--------------------

Submission link: <https://forms.office.com/r/TriiTgFhdC>

Answer all questions given below, each question contains **3 marks**

- 1) Design a **n-bit** Adder/ Subtractor circuit, where collect the value from your ID , consider ID is XX-XXXX**n**-X.
- 2) If your ID is XX-XX**ABC**-X, then explain the working principle of bus organization where the number of registers is **Y=A+B+C** in a micro-operation $R1=R2-R0+5$.
- 3) Now, based on question number 2, design and explain the working process of scratchpad memory and a two-port memory system.
- 4) Explain the process of control logic design including all steps for a signed addition function only.
- 5) Explain the process of control logic design including all steps for a signed subtraction function only.
- 6) Deduce a flowchart and microinstruction table for counting the number of 1's in register **R_A** and storing the count in register **R_B**. Include the values of A and B from your ID if it is XX-XXXX**AB**-X.
- 7) Deduce a flowchart and microinstruction table for counting the number of 0's in register **R_A** and storing the count in register **R_B**. Include the values of A and B from your ID if it is XX-XXXX**AB**-X.



American International University – Bangladesh

Faculty of Engineering – Electrical & Electronics Engineering

8) For the processor unit with 16-bit control word variable as in table below, deduce the control words (using table from question no 10) for the following listed micro-operations:

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
A			B			D			F			Cin	H		

i) $R2 \leftarrow SHL (R3 \text{ OR } R6)$

ii) $R4 \leftarrow 1$

iii) $R3 + \overline{R5} + 1$

iv) $R4 \leftarrow \text{input}$

v) $R4 \leftarrow CLC R2$

9) Design a 4-bit shifter from the given table of question number of 10.

10) Design a 4-bit ALU using table below [consider A & B as ALU source selection, F as the ALU function selection, D as the destination selection and H as shift operation selection variables]

Binary Code	Function of selection variables					
	B	A	F with $C_{in} = 0$	F with $C_{in} = 1$	D	H
				1		
000	Input Data	Input Data	A-1	A	None	-
001	R1	R1	A-B-1	A-B	R1	No shift
010	R2	R2	A+B	A+B+1	R2	Circulate-Right with Carry
011	R3	R3	A	A+1	R3	0's to the output Bus
100	R4	R4	A'	A'	R4	Shift Right with $I_R = 0$
101	R5	R5	A XOR B	A XOR B	R5	Shift Left with $I_L = 0$
110	R6	R6	A U B	A U B	R6	Circulate-Left with Carry
	R7	R7	$A \cap B$	$A \cap B$	R7	1's to the output Bus

Name: MD Abdul Aziz

Section: M

ID : 22-47013-1

Answer to the question no-1

My student ID : 22-47013-1

So, a 3 bit adder/subtractor circuit is given below:

 


Fig: 3 bit adder/subtractor circuit

Ans to the question no-2

My student ID : 22-47013-1

Here, $A=0$, $B=1$, $C=3$

$$\begin{aligned}\therefore Y &= A+B+C \\ &= 0+1+3 \\ &= 4\end{aligned}$$

\therefore A bus organization with $Y=4$ registers, each register is connected to 2 multiplexers to form 2 buses A and B to perform $R_1 = R_2 - R_0 + 5$

- (1) MUX A selector: to Place the Contents of R_2 onto bus A.
- (2) MUX B selector: to Place the contents of R_0 onto bus B
- 3| ALU function selector: to Provide the arithmetic operation A-B
- (4) Shift selector: for direct transfer from the output of the ALU onto output bus S (no shift)
- (5) Decoder Destination selector: to transfer the contents of bus S into R_1 .
- (6) value Addition: Add the value 5 to the result. The operation is done before it is stored in R_1 .

Ans to the question no-3

Based on question number 2, the working Process scratch and a two-Port memory system is given below:

The operation: $R_1 = R_2 - R_0 + 5$

In order to perform the operation binary selection variables must be provided to following sequence.

 


Fig: ScratchPad Memory

T1: $A \leftarrow M[010]$ read the contents R2 into register A

T2: $B \leftarrow M[000]$ read the contents R0 into register B

T3: $C \leftarrow A - B$ Performs the subtraction of the contents of A and B in the ALU storing the results in a temporary register C.

T4: $C \leftarrow C + 5$ add the immediate value 5 to the contents of the temporary register C.

T5: $M[001] \leftarrow C$ transfer the final result from the temporary register C to register R1.

2-Port memory

When $CP=1$, A and B latches are open, accepting information from memory. The WE is also high state. A and B addresses are read from memory and placed into A and B registers.

When $CP=0$, the latches are closed, retaining the last data entered. The control unit provides the necessary signals to perform the subtraction operation in the ALU.

 


Fig: Processor unit with a 2-Port memory

$C \leftarrow C+5$, the Control unit Provides the necessary signals to add with the immediate value. When $CP=0$, the result of the micro-operation is written into memory word defined by B address and then the state of WE is Low and ME is enabled. The necessary signals to store the result in R1 memory address (001) is provided by the Control unit.

Answer to the question no-4

The control logic design process for signed number addition involves creating a complete system that performs binary addition while managing overflow conditions. The steps for a signed addition function is given below:

(1) Understanding Problem Statement: To understand the motive of designing control logic for adding two signed binary numbers and to handle the overflow.

(2) Defining Inputs and outputs: Input includes two signed binary numbers and that results in the result of the operation while an overflow flag also can be generated.

(3) Adder circuit Designing: The inputs to be added by an n -bit adder.

(4) overflow Detection: There are some scenarios when the overflow occurs such as if both operands are positive, but the result is negative or both operands are negative but the results are positive.

(5) Control Signal Implementation: The inputs must be selected. overflow flag should trigger when overflow happens

(6) verification: The accuracy of the sum is verified.

(7) Hardware Implementation: Hardware must be implemented with proper apparatus and connections.

(8) Performance Analysis: Timing analysis must be conducted to ensure the design operates within required time.

Ans to the question no - 5

The Control logic design Process for signed number subtraction involves creating a complete system that performs binary subtraction. The step by step explanation of the control logic design for signed subtraction is given below:

(1) Understanding the Problem Statement:

to understand the motive of designing control logic for subtracting two signed binary numbers.

(2) Defining Inputs and outputs:

Input(A,B) includes two signed binary numbers and that is ~~shown~~ in the result in the result of the operation while an overflow flag also can be generated. The output would be, $R = A - B$

(3) Subtraction Process: subtraction is converted to addition by taking the two's complement of B. Subtract B from A by calculating two's complement of B ($A +$)

(4) Adder Circuit Design: A n-bit adder is used to add A and the two's complement of B.

(5) overflow Detection: There are some scenarios when the overflow occurs such as if the result exceeds the representable range or if the minuend and the subtrahend have different signs but the result has the wrong sign.

(6) Control sign implementation: The inputs must be selected, controls should be enabled when the operation starts and signal overflow must be monitored.

(7) Simulation: subtraction operation is simulated and tested with different inputs.

(8) Hardware Implementation: The logic is implemented in HDL and to verify functionality, the design is mapped.

(9) Timing Analysis: Timing analysis is conducted to ensure the design operates within required time.


Ans to the question no-6

My student ID: 22-47013-1

$$\therefore A=1, B=3$$

Register R_1 contains a binary value (~~$R_1=00000$~~)
($R_1=00000001$) and R_3 will store the count

Flowchart:

 

Microinstruction table of 1's

R1 (Binary)								C	R3(D)
0	0	0	0	0	0	0	1	0	0
0	0	0	0	0	0	0	0	1	1

Ans to the question no - 7

My student ID: 22-47013-1

Here, $A=1$, $B=3$

Register R1 Contains binary value ($R1=00000001$)

Register R3 will store the count of 0's.

Flowchart:



Microinstruction table for 0's

R1 (Binary)								C	R3 (D)
0	0	0	0	0	0	0	1	0	0
1	0	0	0	0	0	0	0	1	0
1	1	0	0	0	0	0	0	0	1
1	1	1	0	0	0	0	0	0	2
1	1	1	1	0	0	0	0	0	3
1	1	1	1	1	0	0	0	0	4
1	1	1	1	1	1	0	0	0	5
1	1	1	1	1	1	1	0	0	6
1	1	1	1	1	1	1	1	0	7


Ans to the question no-8

The Processor Unit with 16-bit control word variable is shown below in the table:

Microoperation	1 2 3	4 5 6	7 8 9	10 11 12	13	14 15 16	
	A	B	D	F	C _{in}	H	Hexa
$R_2 \leftarrow \text{SHL}(R_3 \text{ OR } R_6)$	011	110	010	110	0	101	$(7965)_{16}$
$R_4 \leftarrow 1$	000	000	100	000	0	111	$(1217)_{16}$
$R_3 \leftarrow R_5 + 1$	011	101	000	010	1	000	$(7928)_{16}$
$R_4 \leftarrow \text{input}$	000	000	100	000	0	000	$(1211)_{16}$
$R_4 \leftarrow \text{CCCR2}$	010	000	100	100	0	110	$(4296)_{16}$

Ans to the question no-9

4-bit shifter design:

 

Answer to the question no-10

S_2	S_1	S_0	C_{in}	Function	X_i	Y_i	Z_i
0	0	0	0	$A-1$	A	1	0
0	0	0	1	A	A	1	1
0	0	1	0	$A-B-1$	A	\bar{B}	0
0	0	1	1	$A-B$	A	\bar{B}	1
0	1	0	0	$A+B$	A	B	0
0	1	0	1	$A+B+1$	A	B	1
0	1	1	0	A	A	0	0
0	1	1	1	$A+1$	A	0	1
1	0	0		\bar{A}	A	1	0
1	0	1		$A \oplus B$	A	B	0
1	1	0		$A \cup B$	$A+B$	0	0
1	1	1		$A \cap B$	$A+\bar{B}$	\bar{B}	0

K-maps

(X_i)

$S_2 S_1 \backslash S_0$	0	1
00	A	A
01	A	A
11	$A+B$	$A+B$
10	A	A

$$X_i = A_i + S_2 S_1 \bar{S}_0 B_i + S_2 S_1 S_0 \bar{B}_i$$

(Y_i)

$S_2 S_1 \backslash S_0$	0	1
00	1	\bar{B}
01	\bar{B}	0
11	0	\bar{B}
10	1	\bar{B}

$$Y_i = \bar{S}_2 \bar{S}_1 \bar{B}_i + \bar{S}_2 \bar{S}_0 B_i + S_2 S_0 B_i \bar{B}_i + S_2 S_1 B_i$$

(Z_i)

$S_2 S_1 \backslash S_0$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	0	0	0
10	0	0	0	0

$$Z_i = \bar{S}_2 C_{in}$$

4-bit ALU Design

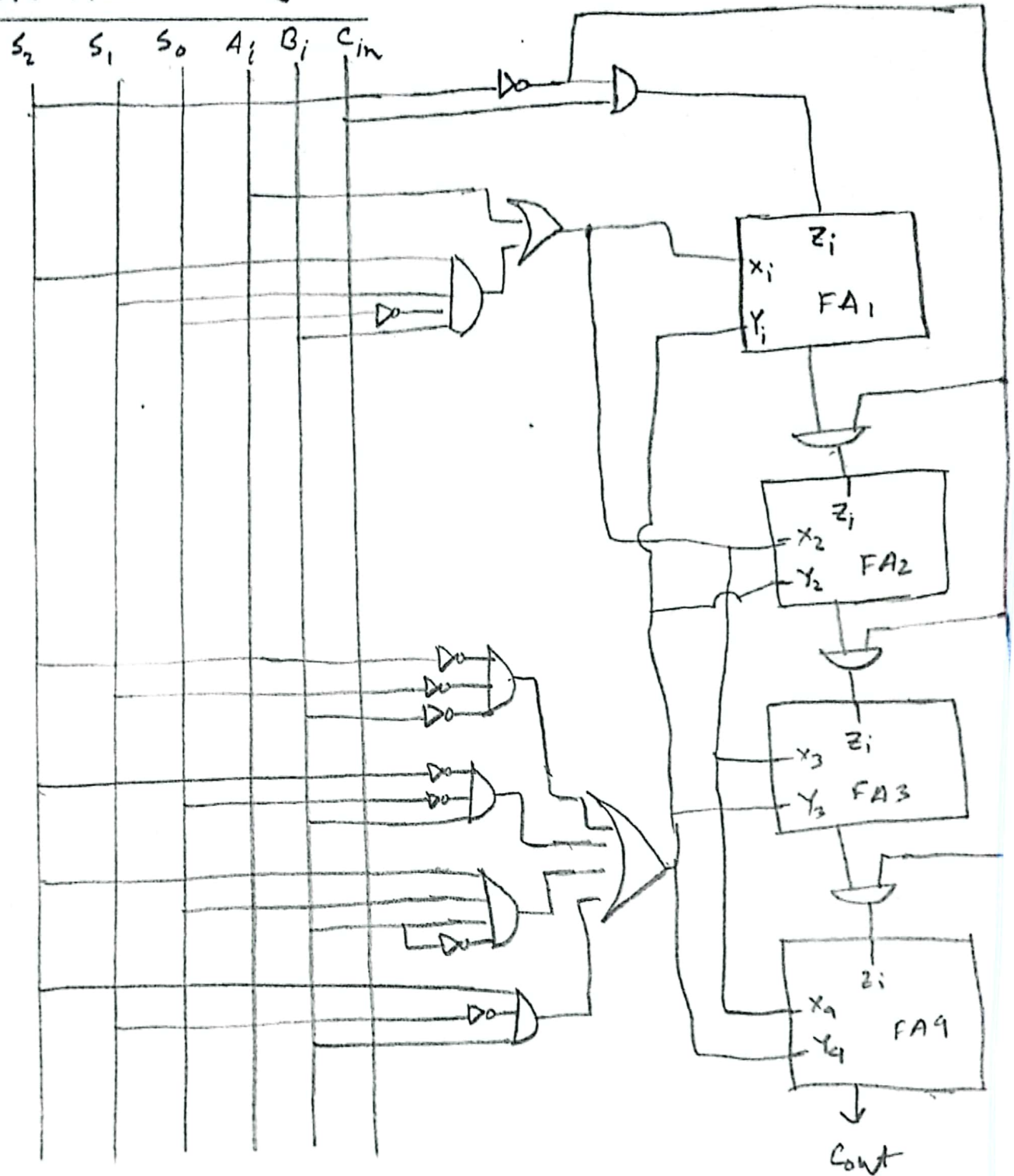


Fig: 4 bit ALU Design